

## DAMPED OSCILLATIONS

If the mass  $m$  be subjected to do damping force proportional to velocity (say:  $c \frac{dx}{dt}$ )

damping force is proportion to the velocity of the mass and acts in the direction opposite to that of motion.

$$m \frac{d^2x}{dt^2} = \text{restoring force} + \text{damping force}$$

$$= -Kx - c \frac{dx}{dt} \quad c \text{ is a positive constant.}$$

$$\Rightarrow m \frac{d^2x}{dt^2} + c \frac{dx}{dt} + Kx = 0$$

$$\text{A.E} \quad m m^{*2} + c m^* + K = 0 \quad m^* = \gamma$$


$$m \gamma^2 + c \gamma + K = 0$$

$$\gamma_1 = \frac{-c + \sqrt{c^2 - 4mK}}{2m}, \quad \gamma_2 = \frac{-c - \sqrt{c^2 - 4mK}}{2m}$$

If  $c^2 - 4mK > 0$  OVER DAMPING

$c^2 - 4mK < 0$  UNDER DAMPING

$c^2 - 4mK = 0$  CRITICAL DAMPING

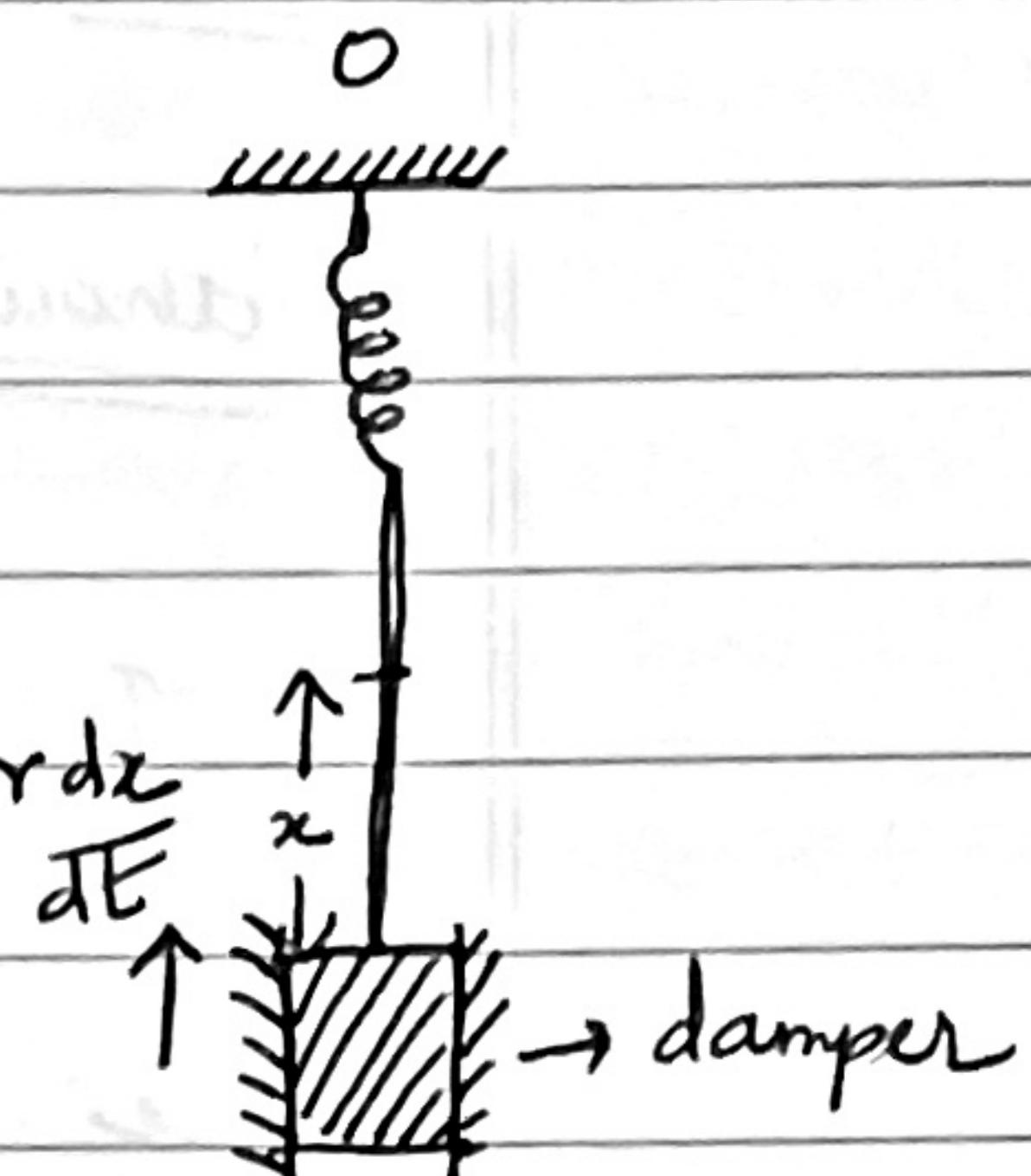

10.0 Newtons = 1.01972

kilograms - factor

## FORCED OSCILLATIONS.

### without damping

If the point of the support of the spring is also vibrating with some external periodic force, the resulting force with motion is called the forced oscillatory motion

$$m \cdot \frac{dx^2}{dt^2} = \text{restoring force} + \text{external force}$$

$$m \frac{d^2x}{dt^2} = -Kx + mp \cos nt$$

$$\frac{d^2x}{dt^2} = -\frac{K}{m}x + p \cos nt$$

Take

$$\boxed{\frac{K}{m} = \mu^2}$$

$$\frac{d^2x}{dt^2} + \mu^2 x = p \cos nt$$

## Forced oscillations (with damping)

$m \frac{d^2x}{dt^2}$  = restoring force + damping force  
+ external periodic force

$$m \frac{d^2x}{dt^2} = -kx - c \frac{dx}{dt} + m p \cos nt$$

$$\frac{d^2x}{dt^2} = -\frac{k}{m}x - \frac{c}{m} \frac{dx}{dt} + p \cos nt$$

Take  $\frac{k}{m} = \mu^2$  and  $\frac{c}{m} = 2\lambda$

$$\Rightarrow \frac{d^2x}{dt^2} + \mu^2x + 2\lambda \frac{dx}{dt} = p \cos nt$$

$$\Rightarrow \frac{d^2x}{dt^2} + 2\lambda \frac{dx}{dt} + \mu^2x = p \cos nt$$

## ELECTRICAL CIRCUIT PROBLEMS

A simple electric circuit used to have a electrical energy source such as a battery, a resistance, a generator etc. This energy is used by the electrical appliances. The source of energy providing an electromotive force (e.m.f)  $E$ , makes a current ( $I$ ) flow through the circuit.

The e.m.f (E), the current (I) and the resistance (R) in a circuit are connected by Ohm's law, which states that  $I \propto E$  (or  $E = IR$ , R is the resistance).

PHYSICAL QUANTITY	SYMBOL	UNIT	DIAGRAMATIC REPRESENTATION
1. e.m.f (or Voltage)	E or V	volt	$\text{---} \parallel \text{---}$
2. current	I or i	ampere	$\rightarrow i$
3. charge	Q or q	coulomb	$\text{---}$
4. resistance	R	ohm	$\text{---} \perp \text{---}$
5. Inductance	L	Henry	$\text{---} \square \text{---}$
6. capacitance	C	Farad	$\text{---} \leftarrow \text{---}$

### L-C Circuits

Consider an electric circuit with an inductance L, a capacitance C. If q is the charge on the capacitor plate and i the current in the circuit at any time t, the voltage drops across the inductance

$$L = L \frac{di}{dt} = L \frac{d^2q}{dt^2} \therefore i = \frac{dq}{dt}$$

(ii) The voltage drop due to capacitance  $= \frac{q}{C}$ .  
 Since there is no applied E.M.F. in the circuit,

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0$$

$$\frac{d^2 q}{dt^2} + \frac{q}{LC} = 0 \quad \frac{1}{LC} = \omega^2$$

$$\Rightarrow \frac{d^2 q}{dt^2} + \omega^2 q = 0.$$

### L-C circuit with an E.M.F

In the previous case, along with inductance L and capacitance C, an e.m.f  $E_0 \cos nt$  is also applied to the circuit, the sum of voltage drops in the circuit equal to the applied e.m.f.

∴ The differential equation becomes.

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = E_0 \cos nt$$

$$\frac{d^2 q}{dt^2} + \frac{q}{LC} = \frac{E_0}{L} \cos nt$$

$$\text{consider } \frac{1}{LC} = \omega^2$$

$$\Rightarrow \frac{d^2 q}{dt^2} + \omega^2 q = \frac{E_0}{L} \cos nt$$

Mech. System

Displacement

Force

Mass m

Damping force

Spring modulus

Series circuit

current i

voltage E

Inductance L

Resistance R

Elastance  $1/c$

7.m.3 as visto duas fo - 3-4