

## L-C circuits

consider an electric circuit containing an inductance  $L$  and a capacitance  $C$ . If  $q$  is the charge on the capacitor plate and  $i$  the current in the circuit at any time  $t$ , then

(i) the voltage drops across the inductance

$$= L \frac{di}{dt} = L \frac{d^2q}{dt^2} \quad \because i = \frac{dq}{dt}$$

(ii) the voltage drop due to capacitance  $= \frac{q}{C}$

since there is no applied emf in the circuit, we have

$$L \frac{d^2q}{dt^2} + \frac{q}{C} = 0$$

$$\Rightarrow \frac{d^2q}{dt^2} + \frac{q}{LC} = 0 \quad \text{Taking } \frac{1}{LC} = \omega^2$$

$$\Rightarrow \frac{d^2q}{dt^2} + \omega^2 q = 0 \quad (\text{Similar to eqn of Free oscillations})$$

## L-C circuit with an emf

In the previous case, along with inductance  $L$  and capacitance  $C$  an emf  $E_0 \cos nt$  is also applied to the circuit, the sum of voltage drops in the circuit equals to an applied emf.


$$\therefore L \frac{d^2q}{dt^2} + \frac{q}{C} = E_0 \cos nt$$



$$\frac{d^2 q}{dt^2} + \omega^2 q = \frac{E_0}{L} \cos \omega t \quad \frac{1}{LC} = \omega^2$$

(Similar to forced oscillations)

case (iii): L-C-R circuit

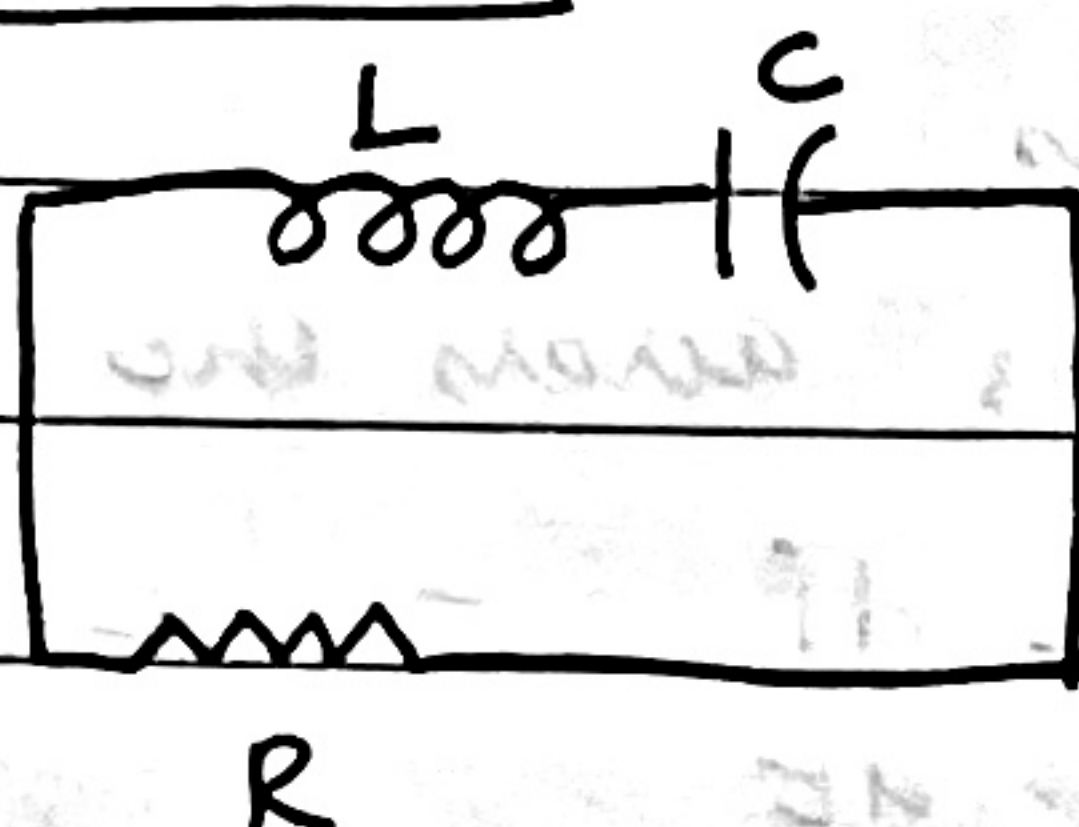

(i) consider a circuit containing an inductance  $L$ , capacitance  $C$  and a resistance  $R$  and  $q$  the charge,  $i$  the current in the circuit at any time  $t$ , then

voltage drops across the inductance  $= L \frac{d^2 q}{dt^2}$

voltage drops due to capacitance  $= \frac{q}{C}$

voltage drop across the resistance  $Ri = R \frac{dq}{dt}$

The governing differential eqn is:

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$


$$\frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0$$

$$\frac{d^2 q}{dt^2} + 2p \frac{dq}{dt} + \omega^2 q = 0 \quad \omega^2 = \frac{1}{LC}, \quad \frac{R}{L} = 2p$$

(Similar to damped oscillations)



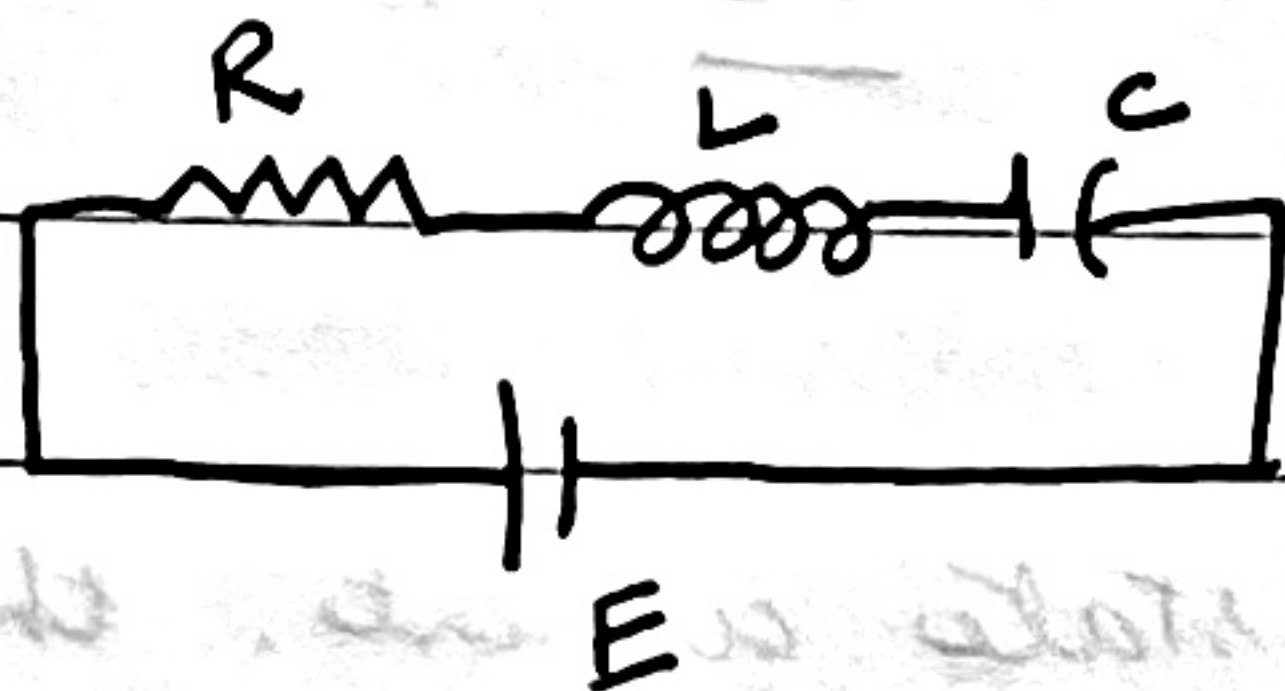case iii L-C-R with emf:  $E_0 \cos nt$ .



By equating the sum of voltage drops to the applied emf the differential eqn can be written as

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = E_0 \cos nt$$

$$\frac{d^2 q}{dt^2} + 2p \frac{dq}{dt} + \omega^2 q = \frac{E_0}{L} \cos nt$$

$$\frac{d^2 q}{dt^2} + 2p \frac{dq}{dt} + \omega^2 q = F \cos nt$$

(similar to forced with  
damping oscillations)

$$\left\{ \begin{array}{l} \frac{1}{LC} = \omega^2 \\ \frac{R}{L} = 2p \\ \frac{E_0}{L} = F \end{array} \right.$$